

LAB 3


Application of Laplace Transforms : Operational
Amplifier Filters.

ECEn 380 Section 001

Task 1 signoff:  10/12

Task 2 signoff:  10/19

10/5/15



Objective

The purpose of this lab is to solidify our understanding of Laplace Transform analysis in circuit design. We are also going to analyze, design, and experimentally verify the functionality of a basic filter design.

Task 1
Step 2

$$\frac{V_i - V_1}{R_1} + \frac{V_0 - V_1}{1/sC_1} + \frac{V_0 - V_1}{R_2} = 0 \quad (1) \quad V_1 = V_0(sC_2R_2 + 1) \quad (2)$$

Substitute V_1 into equation (1)

$$\frac{V_i - V_0 - V_0sC_2R_2}{R_1} + \frac{V_0 - V_0 - V_0sC_2R_2}{1/sC_1} + \frac{V_0 - V_0 - V_0sC_2R_2}{R_2} = 0$$

$$\frac{V_i}{R_1} - \frac{V_0}{R_1} - \frac{V_0sC_2R_2}{R_1} - V_0s^2C_1C_2R_2 - V_0sC_2 = 0$$

$$\frac{V_i}{R_1} = \frac{V_0}{R_1} + \frac{V_0sC_2R_2}{R_1} + V_0s^2C_1C_2R_2 + V_0sC_2 = 0$$

$$\frac{V_i}{R_1} = V_0 \left(\frac{1}{R_1} + \frac{sC_2R_2}{R_1} + s^2C_1C_2R_2 + sC_2 \right)$$

$$\frac{V_i}{R_1} = V_0 \left(s^2C_1C_2R_2 + s \left(C_2 + \frac{C_2R_2}{R_1} \right) + \frac{1}{R_1} \right)$$

$$\frac{\left(\frac{1}{C_1C_2R_2} \right) \frac{1}{R_1}}{\left(\frac{1}{C_1C_2R_2} \right) s^2C_1C_2R_2 + s \left(C_2 + \frac{C_2R_2}{R_1} \right) + \frac{1}{R_1}} = \frac{V_0}{V_i} = \boxed{\frac{1}{R_1R_2C_1C_2}} = H(s)$$

Step 3

$$\begin{aligned} & \omega_c^4 \quad H_1(s) H_2(s) \\ & (s - \omega_c e^{j\frac{5}{8}\pi})(s - \omega_c e^{-j\frac{5}{8}\pi})(s - \omega_c e^{j\frac{7}{8}\pi})(s - \omega_c e^{-j\frac{7}{8}\pi}) \\ & = \frac{\omega_c^2}{(s - \omega_c e^{j\frac{5}{8}\pi})(s - \omega_c e^{-j\frac{5}{8}\pi})} \cdot \frac{\omega_c^2}{(s - \omega_c e^{j\frac{7}{8}\pi})(s - \omega_c e^{-j\frac{7}{8}\pi})} \\ & \quad \begin{array}{c} 1 \\ H_1(s) \end{array} \quad \begin{array}{c} 1 \\ H_2(s) \end{array} \\ & \quad \begin{array}{c} 1 \\ \omega_c^2 \end{array} \quad \begin{array}{c} 1 \\ \omega_c^2 \end{array} \\ & \frac{\omega_c^2}{s^2 + \sqrt{2-\sqrt{2}} s \omega_c + \omega_c^2} \quad \frac{\omega_c^2}{s^2 + \sqrt{2+\sqrt{2}} s \omega_c + \omega_c^2} \\ & H_1(s) \approx \frac{\omega_c^2}{s^2 + 0.7654 \omega_c s + \omega_c^2} \quad H_2(s) \approx \frac{\omega_c^2}{s^2 + 1.8478 \omega_c s + \omega_c^2} \end{aligned}$$

$$\begin{aligned} H_1(s) \quad \omega_c &= 2\pi(3 \times 10^3) \\ H_1(s) &= \frac{3.553 \times 10^8}{s^2 + 14427s + 3.553 \times 10^8} \end{aligned}$$


$$H_2(s) = \frac{3.553 \times 10^8}{s^2 + 34830s + 3.553 \times 10^8}$$

10/5/15

Benjamin Bergeron

to Sample code: $B = [0, 0, 5, 2];$
 $A = [1, 3, 0, 4];$
 $zplane(B, A);$


SAMPLE GRAPH

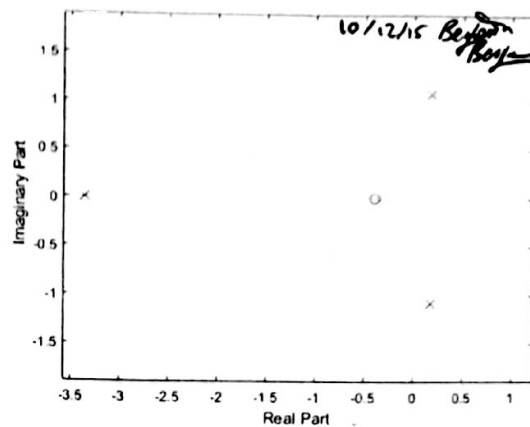

Task 1 step 4

Our Code: $A1 = [1, 14427, 3.553e8];$
 $A2 = [1, 34830, 3.553e8];$
 $A = \text{conv}(A1, A2);$
 $B1 = [3.553e8];$
 $B2 = [3.553e8];$
 $B = \text{conv}(B1, B2);$
 $zplane(B, A);$

Our Graph

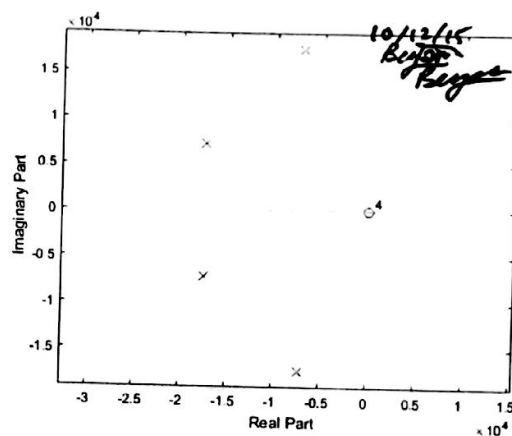

Our code for Bode plot.

$A1 = [1, 14427, 3.553e8];$
 $A2 = [1, 34830, 3.553e8];$

10/12/15 Benjam Bergeron

$A = \text{conv}(A1, A2);$

$B1 = [3.553e8];$

$B2 = [3.553e8];$

$B = \text{conv}(B1, B2);$

%creates a vector with 500 points between 0 and 5 that are logarithmically
 %equally spaced

$f = \text{logspace}(0, 5, 500);$

%creates a Laplace Transform frequency plot evaluated at $2\pi f$

$[H, w] = \text{freqs}(B, A, 2\pi f);$

%plots x axis logarithmically and y normally.

$\text{semilogx}(f, 20 \cdot \log_{10}(\text{abs}(H)))$


$\text{xlabel}('Frequency in Hz');$ %labels the x axis

$\text{ylabel}('Magnitude response in dB');$ %labels the y axis

Task 1 Step 5

10/12/15
 Benjam Bergeron


Task 1 step 5

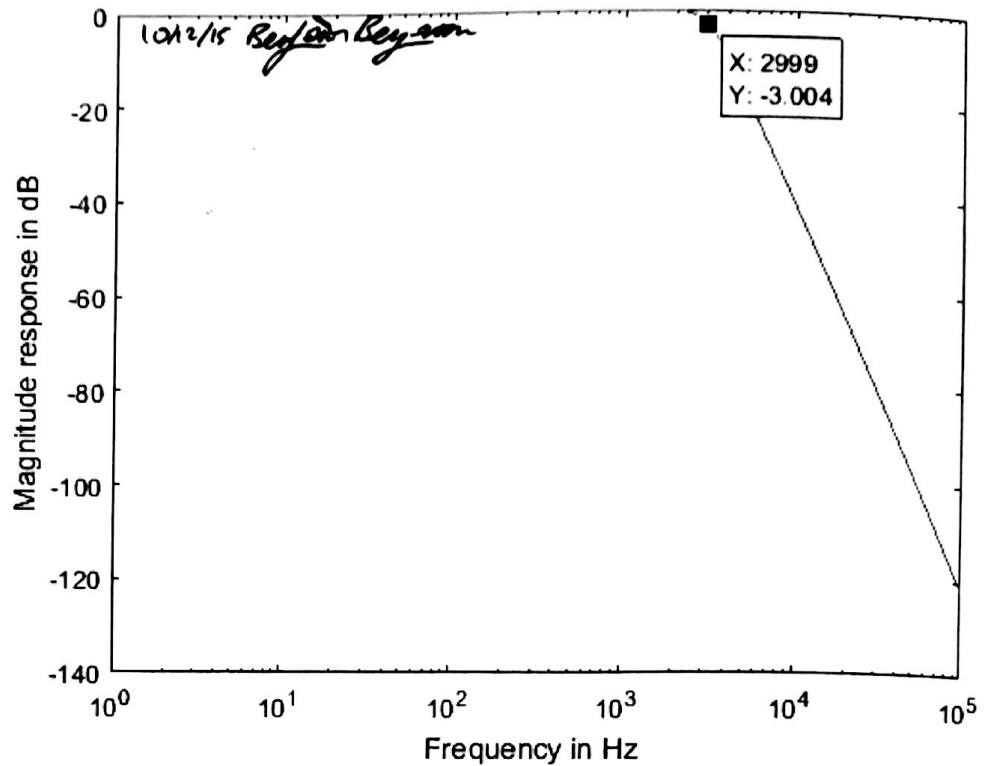

Task 1 step 6

$H(s) = H_1(s) \cdot H_2(s)$ because convolution in the time domain is multiplication in the s-domain.

Task 1 step 7

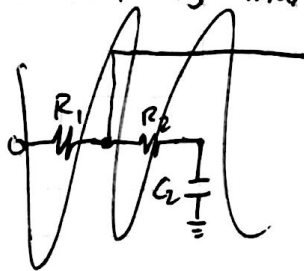

$$\text{For } H_1(s): \frac{1}{C_1 C_2 R_1 R_2} = 3.553 \times 10^8 = \frac{1}{(1k)(1k)C_1 C_2}$$

$$\frac{1}{C_1 R_1} + \frac{1}{C_1 R_2} = 14427 = \frac{1}{(1k)C_1} + \frac{1}{(1k)C_1}$$

$$\boxed{C_1 = 1.386 \times 10^{-7} = 0.1386 \mu F}$$

$$\boxed{C_2 = 2.03 \times 10^{-8} = 0.0203 \mu F}$$


$$\text{For } H_2(s): \frac{1}{(1k)(1k)C_1 C_2} = 3.553 \times 10^8$$

$$\frac{1}{(1k)C_1} + \frac{1}{(1k)C_1} = 34830$$

$$\boxed{C_1 = 5.74 \times 10^{-8} = 0.0574 \mu F}$$

$$\boxed{C_2 = 4.9 \times 10^{-8} = 0.049 \mu F}$$

10/12/15
Raydon Beynon

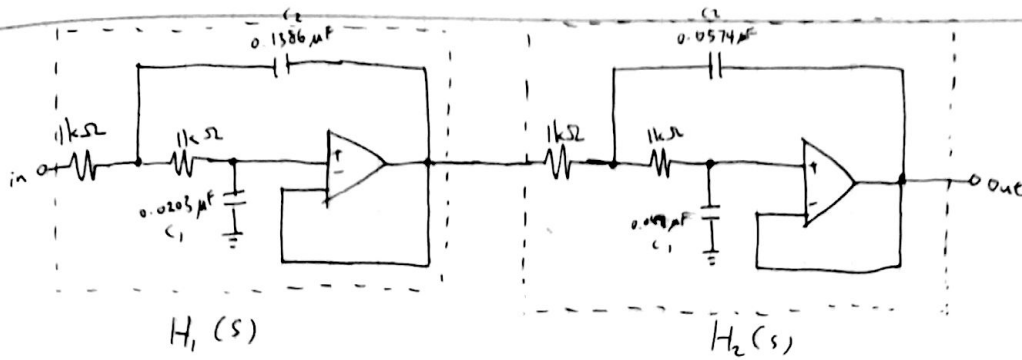


Actual capacitor values: $H_1(s)$: $C_1 = 138\text{nF}$ $C_2 = 24\text{nF}$ $H_2(s)$: $C_1 = 57\text{nF}$ $C_2 = 48\text{nF}$

It attenuates higher frequencies. When measuring each of the filters individually, they don't attenuate as much as when they are cascaded together. When using speech alone as an input, the words come through fine, but at a lower volume. We noticed that when playing music as the input, some of the higher notes get attenuated.

Task 2 Step 1

Task 2 Step 2

Phase Response for cascaded filters

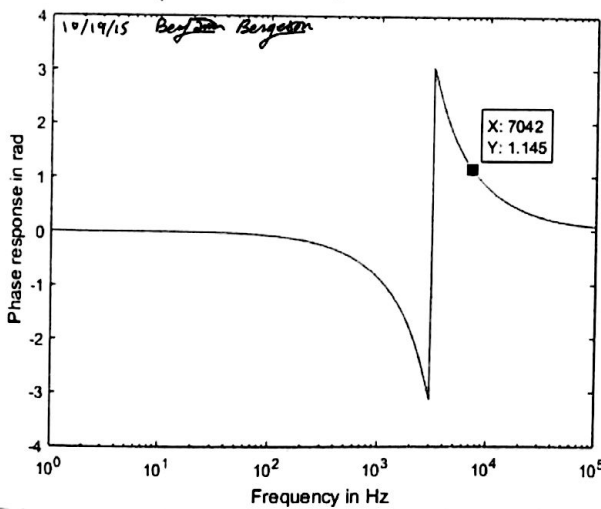


The magnitude frequency response can be seen on page 26.

The MATLAB simulation yielded the following results:

- @ 20 Hz: 0 rad $\approx 0^\circ$
- @ 1 kHz: -0.8983 rad $\approx -51.47^\circ$
- @ 3 kHz: $-\pi$ rad $\approx -180^\circ$
- @ 5 kHz: 1.67 rad $\approx 95.68^\circ$
- @ 7 kHz: 1.145 rad $\approx 65.6^\circ$

Task 2 Step 3 for cascaded filters

@ 20 Hz

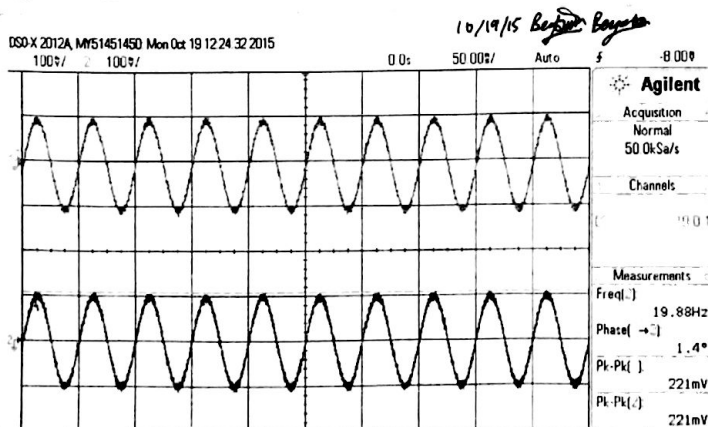

Measured phase = $1.40 \approx 0^\circ$

Measured Gain = 0

The measured phase and magnitude are very similar to the MATLAB simulation.

Calc Gain: 0


Task 2 Step 3 for cascaded filters

10/19/15

Beyza Beyza

Task 2 step 4
for cascaded filters

@ 1 kHz

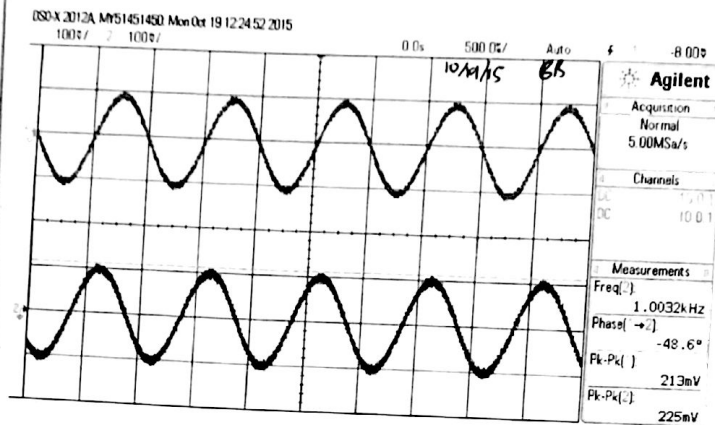


Measured phase: -48.6°
Measured Mag. ≈ 0

Fairly close to phase of -54.4°

Calc Gain: -6.9×10^{-4}

@ 3 kHz

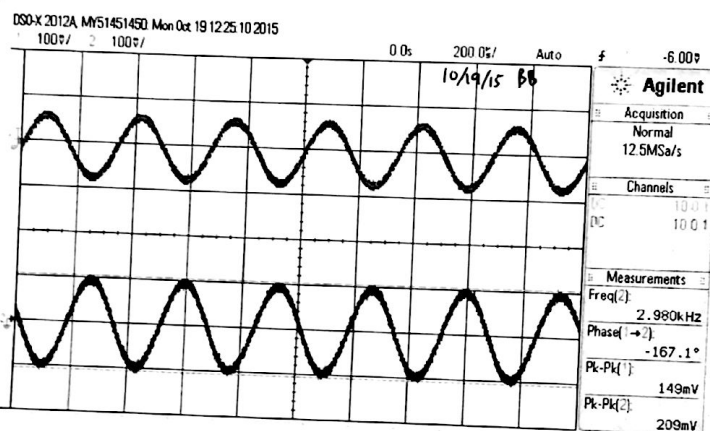


Measured phase: -167.1°
Calc. phase: -180°

Measured Gain: -2.9

Calc Gain: -3

@ 5 kHz

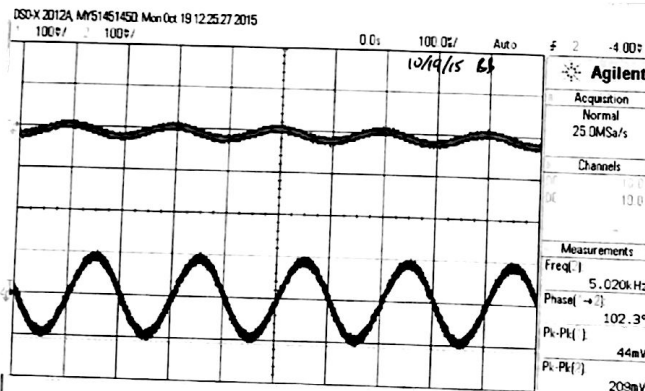


Meas. phase: 102.3°
Calc phase: 95.68°

Meas. Gain: -13.57

Calc Gain: -17.7

@ 7 kHz

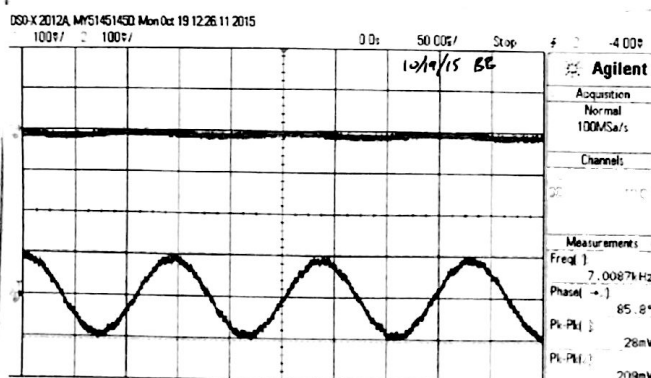


Meas. phase: 85.8°
Calc. phase: 65.6°

Meas. Gain: -17.5

Calc Gain: ≈ -24

10/26/15

Benjamin Bergeron

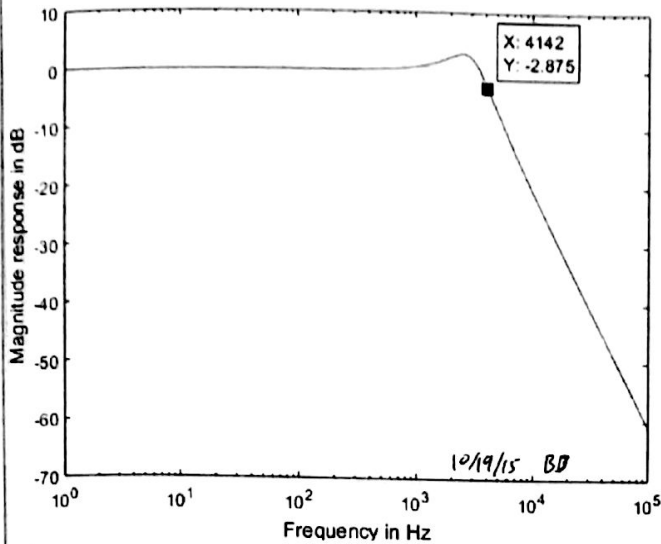


Corner Frequency.

- @ 20 Hz : 0
- @ 1 kHz : 0.67
- @ 4.3 kHz : -3
- @ 5 kHz : -7
- @ 7 kHz : -13.5

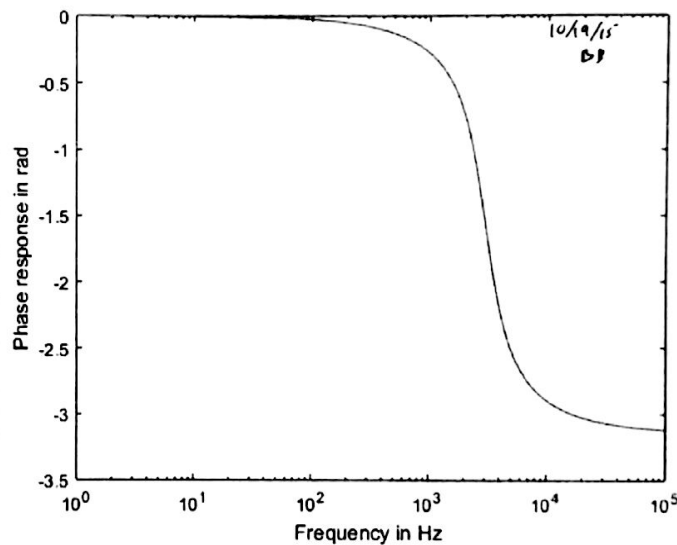
Task 2 steps
for single filter

Phase Shift:

- @ 20 Hz : $-0.2765 \text{ rad} = 0^\circ$
- @ 1 kHz : $-0.2765 \text{ rad} = -15.8^\circ$
- @ 4.3 kHz : $-2.3 \text{ rad} = -131.8^\circ$
- @ 5 kHz : $-2.516 \text{ rad} = -144.1^\circ$
- @ 7 kHz : $-2.76 \text{ rad} = -158.1^\circ$



@ 20 Hz

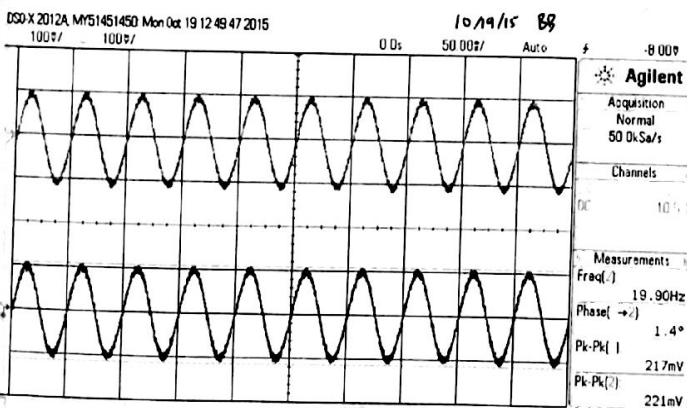Measured Phase : $1.4^\circ \approx 0$


Calc. Phase : 0

Measured Gain : -0.16

Calc. Gain : 0

Task 2 Step 4
for single filter

@ 1 kHz

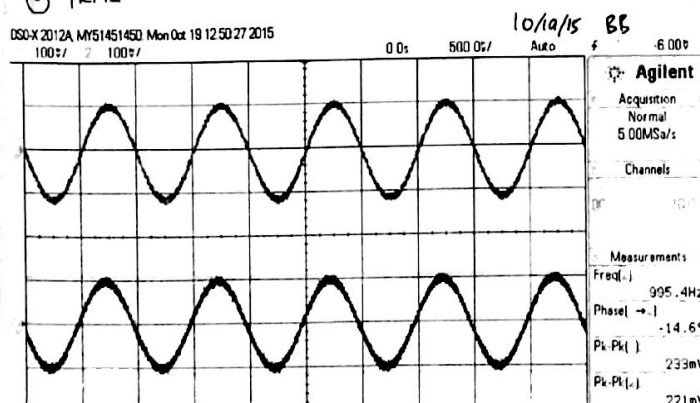Measured Phase : -14.6° Calc. Phase : -15.8°

Measured Gain : 0.46


Calc. Gain : 0.67

10/26/15

Benjamin Baye

Task 2 step 4
for single filter


Ⓐ 4.3 kHz

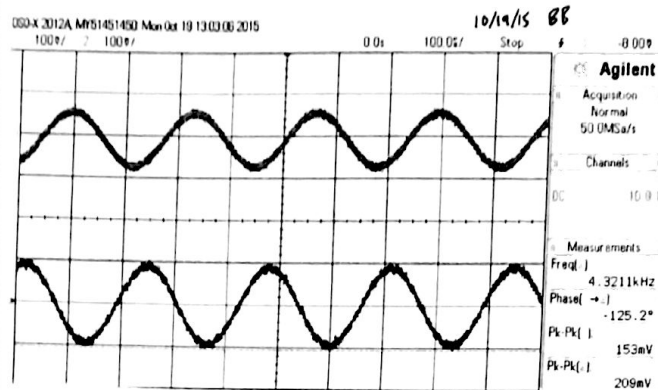

Measured Phase: -125.2°
Calc Phase: -131.8°

Measured Gain: -2.7
Calc Gain: -3


Ⓑ 5 kHz

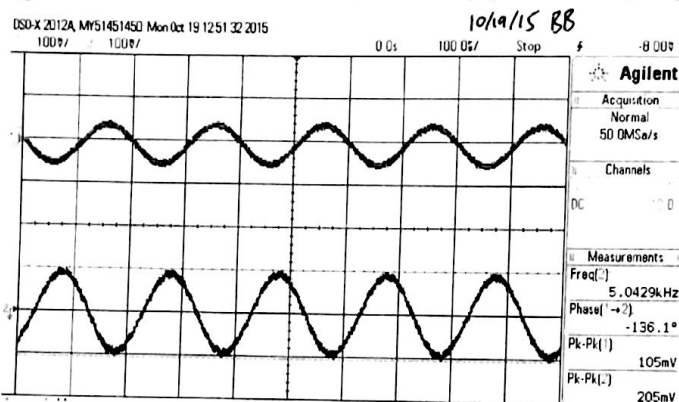

Measured Phase: -136.1°
Calc Phase: -144.1°

Measured Gain: -5.8
Calc Gain: -7

Ⓒ 7 kHz

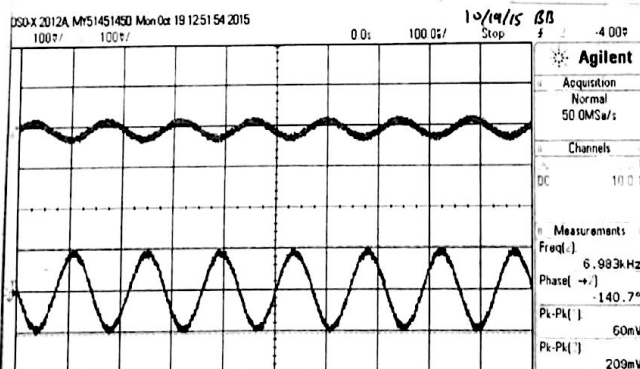

Measured Phase: -140.7°
Calc. Phase: -158.1°

Measured Gain: -10.8
Calc Gain: -13.5

In both the cascaded filters & the single filter, it seems that larger the frequency, the larger the discrepancies between measured values and calculated values.

10/26/15

Benjamin Bergeron

Conclusion

In this lab we were able to design a Butterworth filter with four poles and no zeros by cascading two Sallen-Key filters. Using KCL we were able to find the transfer function of the individual Sallen-Key filters. Knowing that this is a fourth order Butterworth filter we're designing, we could figure out the transfer function. All that's left is to solve algebraically for the values of the resistors and capacitors of the two Sallen-Key filters. Using those values we were able to plot the poles and zeros in MATLAB using the `zplane` command.

Using these calculated values, we were able to simulate the frequency response for magnitude and the frequency response for phase for the ~~cascaded filters as~~ Butterworth filter and one of the Sallen-Key filters. We were then able to physically build the circuit and measure the outputs with the oscilloscope.

There were some small ~~errors~~ ^{discrepancies} between the simulated values and the actual measured values. The phase shifts were relatively close, with the margin of error being around 10% max. However we noticed that our physical circuit would not attenuate as much as the simulated circuit. However the corner frequencies were very close. We think that some of the error could be due in part to the fact that the capacitor value we chose weren't exactly the values that we calculated.

Overall, this was a very educational experience in learning how to build a low pass Butterworth filter from scratch.

Conclusion